



midterm review: sds

ta: sophie xie

credit to: su24 61c, nikhil kandkur, erik yang, andrew liu


3 types of components

  - combinational logic
 - output changes based on inputs after x seconds of delay
- state elements (e.g. registers)
 - output changes according to the clock signal; remembers input even after input changes due to the output only changing according to the clock
- clock
 - ticks at steady rate going from 0→1→0→1... etc.



registers

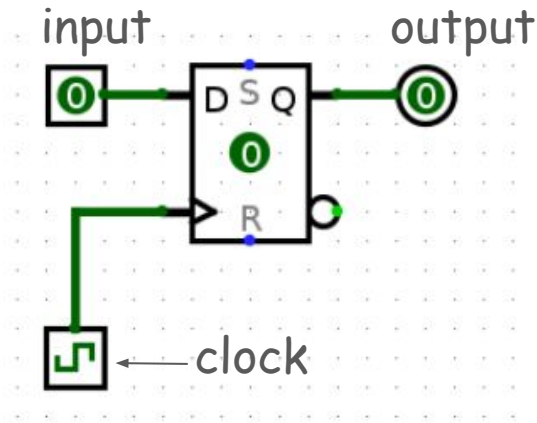- a **register** is a small and fast storage object that is controlled by a clock
- at the **rising edge** of the clock, the output updates to match the input
- at all other times, the output remains constant regardless of input value





some helpful definitions:

- **rising clock edge**: when the clock goes from 0 → 1
- **falling clock edge**: when the clock goes from 1 → 0


registers, more definitions

- **setup time:** time before the rising edge of the clock in which the input must be stable
- **hold time:** time after the rising edge of the clock in which the input must be stable
- **clock-to-q delay:** time it takes for the register's input to become its output after the rising edge of the clock
- **clk-to-q delay \geq hold time:** if it takes clk-to-q to propagate value, why have a longer hold time?

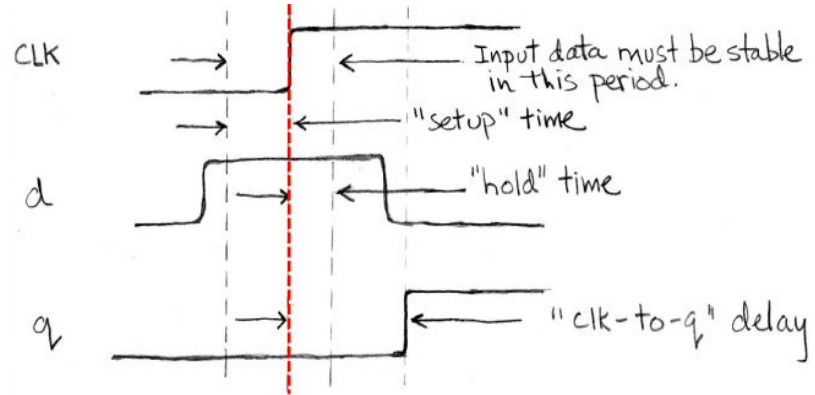 

more definitions

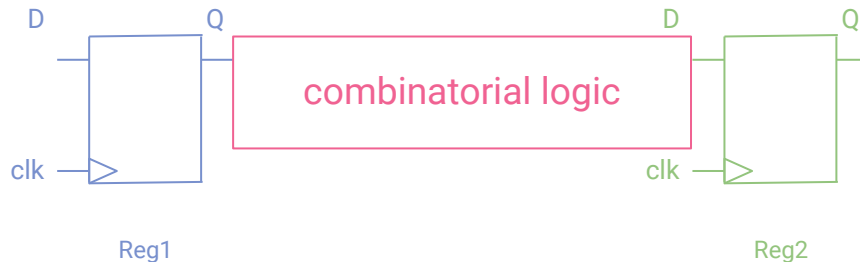- **combinational logic delay**
 - combinatorial delay between 2 state elements
- **critical path:**
 - longest delay between 2 state elements
 - clock period must be longer than critical path
- **minimum clock period (ns) = critical path**
- **maximum clock frequency (Hz) = $1/(\text{min. clk period}) = 1/CP$**



$$CP = \text{clk-to-q} + \text{longest CL delay} + \text{setup time}$$

Reg1 max(for all sum(all in-series CL delays)) Reg2

important formulas (put on cheatsheet!)

$$t_{\text{clk-to-q}} + t_{\text{shortest-combinational-path}} \geq t_{\text{hold}}$$

$$t_{\text{clk-to-q}} + t_{\text{longest-combinational-path}} + t_{\text{setup}} \leq t_{\text{clk-period}}$$

Max hold time: Signal feeding into the register needs to be stable long enough after clock tick, and the shortest path might affect that

Min clock period: Want to guarantee that the entire circuit is stable before we start the next clock cycle.

A circuit must fulfill these conditions in order to exhibit consistently correct behavior

Satisfying Hold Time Constraints

- Hold time constraint:

Hold time \leq clk-to-q delay + shortest combinational path

- After the rising edge, we have to wait clk-to-q seconds for the Q output to change
- Then, after the shortest combinational path, one of the D inputs will change
- We need the hold time to be over by the time the D input changes

Maximizing Clock Frequency


- Setup time and combinational delay constraint:

Clock period \geq clk-to-q delay + longest combinational path + setup time

- After the rising edge, we have to wait clk-to-q seconds for the Q output to change
- Then, we have to wait for the longest combinational path for the result to appear at the D input
- Then, we have to hold that D input stable for the setup time

FA21 Final Q4

 Consider the following circuit. Assume that AND and OR gates have a delay of 8 ps (picoseconds), NOT gates have a delay of 4 ps, and all registers have a setup time constraint of 6 ps and clock-to-Q delay of 3 ps. Assume all wires are ideal, i.e. they have zero delay.



FA21 Final Q4

- a. What is the largest combinational delay of all paths in this circuit, in picoseconds?

$$16 \text{ ps} = 8 \text{ (AND)} + 8 \text{ (OR)}$$

- b. What is the smallest combinational delay of all paths in this circuit, in picoseconds?

$$12 \text{ ps} = 4 \text{ (NOT)} + 8 \text{ (AND)}$$

- c. What is the maximum possible hold time constraint for registers to function properly in this circuit, in picoseconds?

$$15 \text{ ps} = 12 + 3 \text{ (c2q)}$$

- d. What is the minimum allowable clock period for this circuit to function properly, in picoseconds?


$$25 \text{ ps} = 16 + 6 \text{ (setup)} + 3 \text{ (c2q)}$$

- e. What is the maximum allowable clock frequency for this circuit to function properly, in gigahertz?

$$40 \text{ GHz} = 1/(25 \text{ ps})$$

SP21 MT Q3

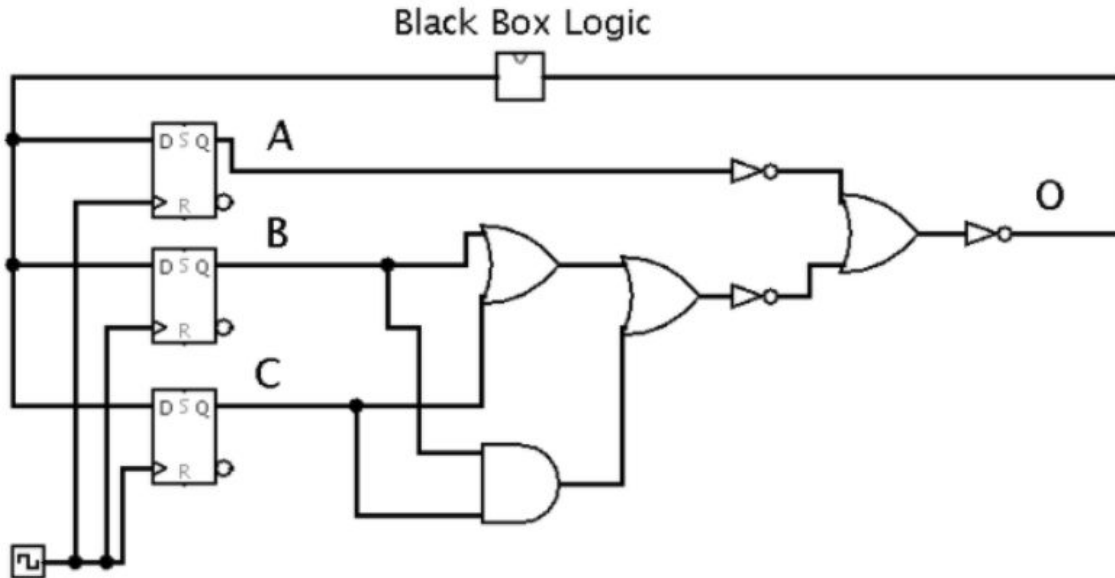In the following circuit, the registers have a clk-to-q delay of 6ns and setup times of 5ns. NOT gates have a delay of 3ns, AND and OR gates have a delay of 7ns, and the “Black Box” logic component has a delay of 9ns.



SP21 MT Q3


a. What is the maximum allowable hold time of the registers?

$$28 \text{ ns} = 6 \text{ (c2q)} + 3 \text{ (NOT)} + 7 \text{ (OR)} + 3 \text{ (NOT)} + 9 \text{ (BBL)}$$

b. What is the minimum acceptable clock period for this circuit?


$$47 \text{ ns} = 6 \text{ (c2q)} + 7 \text{ (AND)} + 7 \text{ (OR)} + 3 \text{ (NOT)} + 7 \text{ (OR)} + 3 \text{ (NOT)} + 9 \text{ (BBL)} + 5 \text{ (setup)}$$

FA23 MT Q5

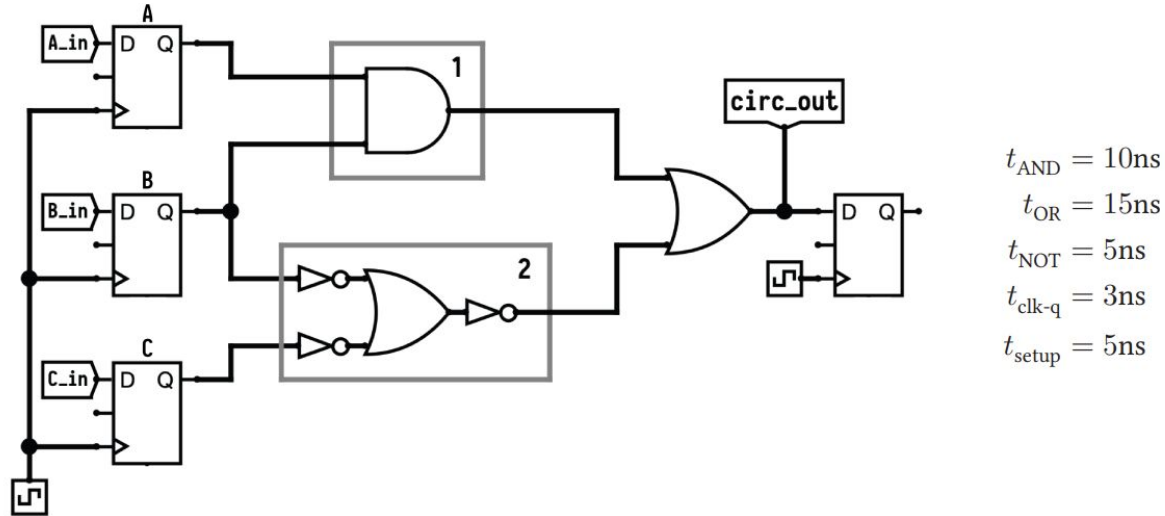

Q5.1 (2.5 points) What is the **minimum clock period**, in nanoseconds, for the circuit above such that it will always exhibit well-defined behavior?


FA23 MT Q5

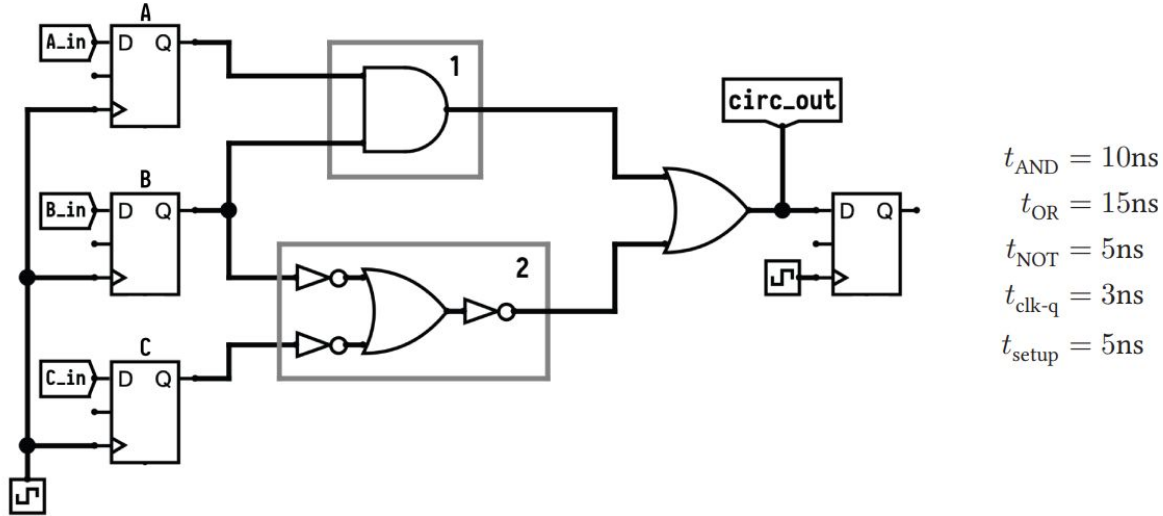

Q5.1 (2.5 points) What is the **minimum clock period**, in nanoseconds, for the circuit above such that it will always exhibit well-defined behavior?


48ns \Rightarrow 3ns (clk-q) + 5ns (NOT) + 15ns (OR) + 5ns (NOT) + 15ns (OR) + 5ns (setup)

FA23 MT Q5

 

Q5.2 (2.5 points) What is the **maximum hold time**, in nanoseconds, for the circuit above such that it will always exhibit well-defined behavior?

FA23 MT Q5

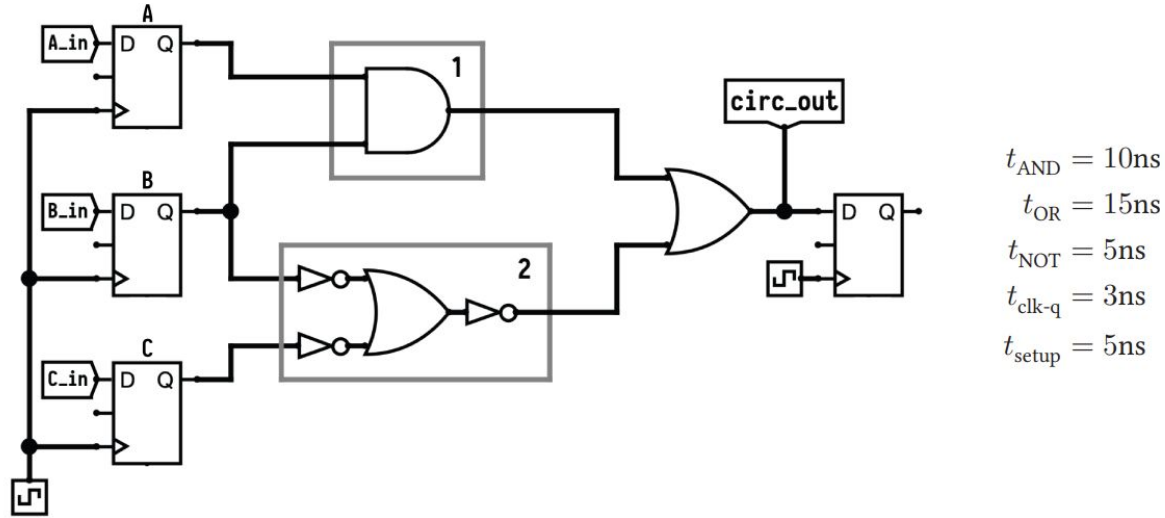


Q5.2 (2.5 points) What is the **maximum hold time**, in nanoseconds, for the circuit above such that it will always exhibit well-defined behavior?

$$28\text{ns} \Rightarrow 3\text{ns (clk-q)} + 10\text{ns (AND)} + 15\text{ns (OR)}$$

FA23 MT Q5


For the rest of this question, consider the updated circuit diagram and timings below. Subcircuits 1 and 2 are black-boxes that compute the Boolean expressions shown in the diagram. Regardless of your previous answers, assume the clock period is 80ns, and for subcircuits 1 and 2, their respective minimum and maximum combinational logic delays are equal. For example, if the input to subcircuit 1 changed at $t = 0$ (and no other changes occur), then the output to subcircuit 1 will change at $t = 13$ only.

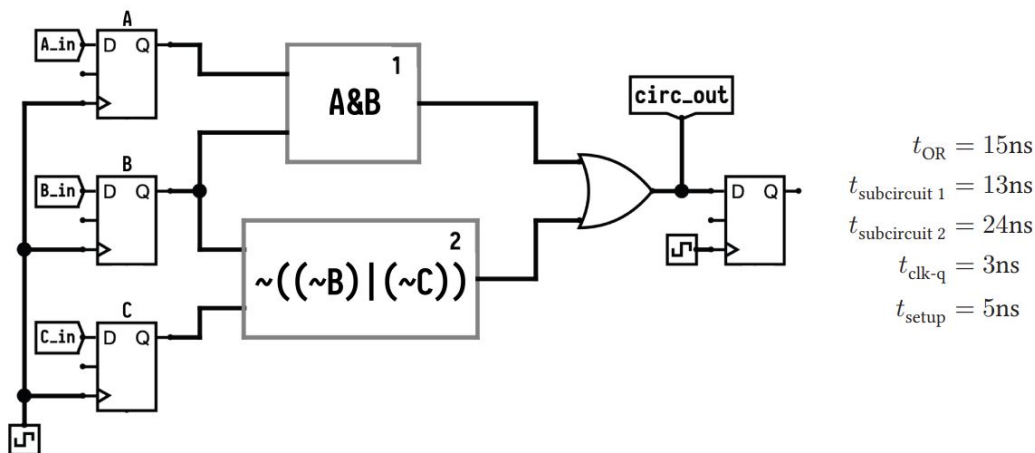

Until this circuit settles at the correct input, it calculates two other Boolean expressions at the tunnel `circ_out`. Assume that register outputs are all 0 at $t = 0$, and that there are no setup or hold time violations.

Q5.3 (2 points) Let t_1 be the first time that `circ_out` changes. What is t_1 in nanoseconds? Clarified during exam: t_1 is the first time that `circ_out` *may change*.


FA23 MT Q5

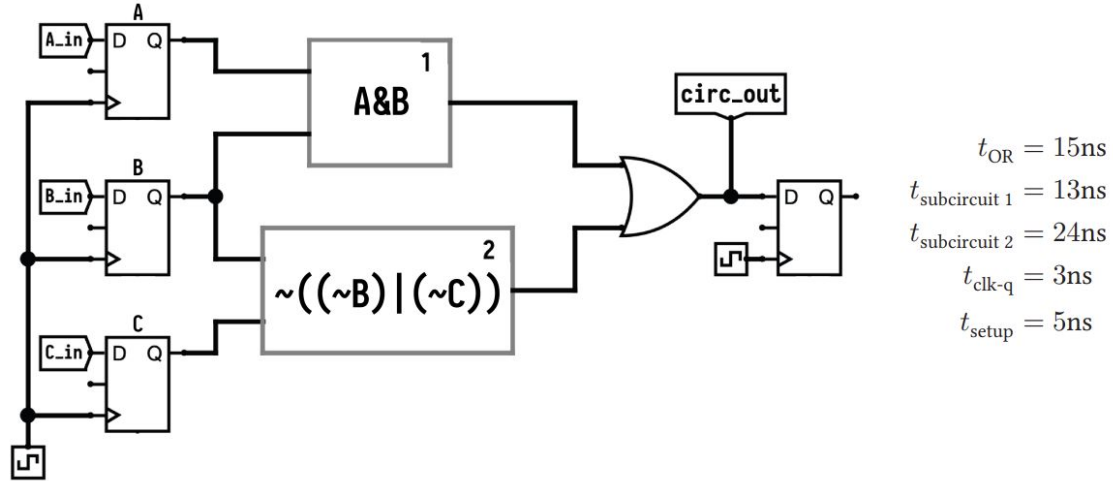

Q5.3 (2 points) Let t_1 be the first time that `circ_out` changes. What is t_1 in nanoseconds? Clarified during exam: t_1 is the first time that `circ_out` *may change*.


$$31\text{ns} \Rightarrow 3\text{ns (clk-q)} + 13\text{ns (subcircuit 1)} + 15\text{ns (OR)}$$

FA23 MT Q5

 

Q5.4 (2 points) Let t_2 be the second time that `circ_out` changes. What is t_2 in nanoseconds?


FA23 MT Q5

 

Q5.4 (2 points) Let t_2 be the second time that `circ_out` changes. What is t_2 in nanoseconds?


$$42\text{ns} \Rightarrow 3\text{ns (clk-q)} + 24\text{ns (subcircuit 2)} + 15\text{ns (OR)}$$

FA23 MT Q5

 

Q5.5 (2 points) What simplified Boolean expression does the circuit calculate while $0\text{ns} \leq t < t_1$?


FA23 MT Q5

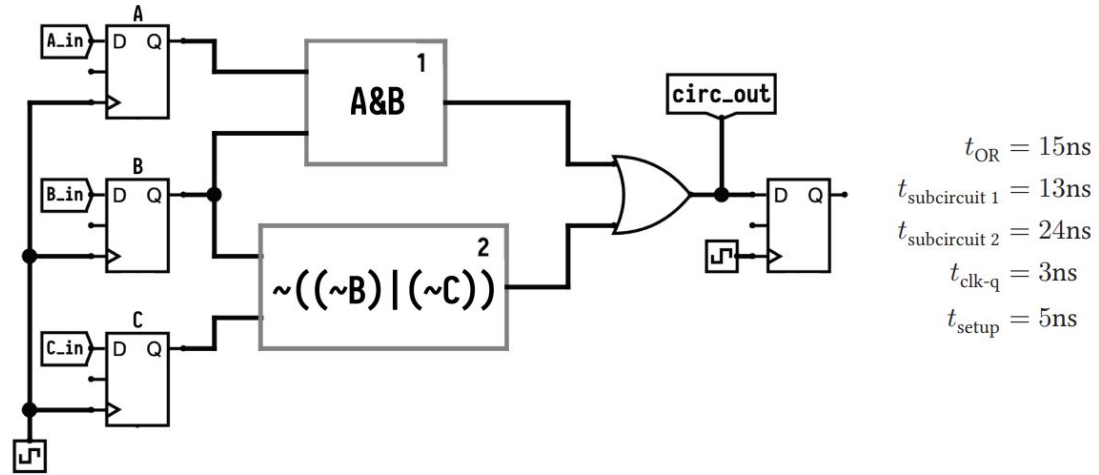

Q5.5 (2 points) What simplified Boolean expression does the circuit calculate while $0\text{ns} \leq t < t_1$?

0, since wires are initialized to 0, the output at circ_out will be 0.


FA23 MT Q5

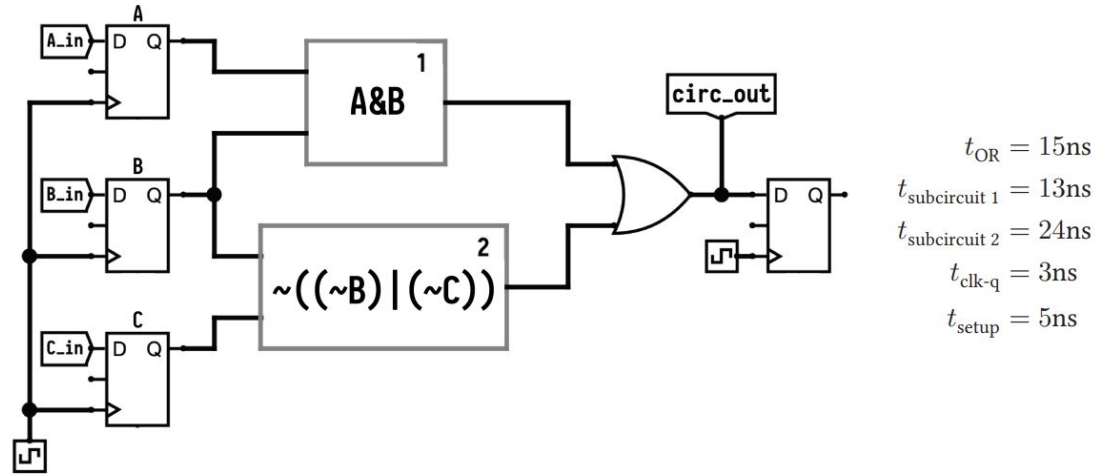

Q5.6 (2 points) What simplified Boolean expression does the circuit calculate while $t_1 \leq t < t_2$?


$A \& B \Rightarrow$ this is the output of subcircuit 1 ORed with 0

FA23 MT Q5

 

Q5.7 (2 points) What simplified Boolean expression does the circuit calculate while $t_2 \leq t < 80\text{ns}$?

FA23 MT Q5

 

Q5.7 (2 points) What simplified Boolean expression does the circuit calculate while $t_2 \leq t < 80\text{ns}$?

$$(A \& B) \mid (\sim((\sim B) \mid (\sim C))) \Rightarrow (A \& B) \mid (\sim(\sim(B \& C))) \Rightarrow (A \& B) \mid (B \& C) \Rightarrow (A \mid C) \& B$$